```
FA:
```

```
ENTITY FA IS PORT (
  a: IN STD LOGIC VECTOR(1 DOWNTO 0);
  b: IN STD_LOGIC_VECTOR(1 DOWNTO 0);
  cin: IN STD_LOGIC;
  r: OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
  cout: OUT STD_LOGIC
);
END FA;
ARCHITECTURE arch OF FA IS
BEGIN
r(1) \le ((a(1) \text{ and not } a(0) \text{ and } b(1) \text{ and not cin}) \text{ or } a(1) \le ((a(1) \text{ and not cin}))
    (a(1) and b(1) and b(0) and cin) or
     (a(1) and a(0) and b(1) and not b(0)) or
    (not a(1) and not a(0) and not b(1) and not cin) or
    (not a(1) and not b(1) and b(0) and cin) or
     (not a(1) and a(0) and not b(1) and not b(0)) or
     (not a(1) and a(0) and b(1) and b(0) and not cin) or
     (not a(1) and not a(0) and b(1) and not b(0) and cin) or
    (a(1) and a(0) and not b(1) and b(0) and not cin) or
    (a(1) and not a(0) and not b(1) and not b(0) and cin)) after 10 ns;
r(0) \le ((a(0) \text{ and not } b(0) \text{ and not cin}) \text{ or }
    (a(0) and b(0) and cin) or
    (not a(0) and b(0) and not cin) or
    (not a(0) and not b(0) and cin)) after 10 ns;
cout <= ((not a(1) and not b(1) and not b(0) and cin) or
     (not a(1) and not a(0) and cin ) or
    (a(0) and b(1) and b(0)) or
    (not a(1) and b(1) and b(0)) or
    (a(1) and a(0) and cin) or
    (not a(1) and not a(0) and not b(1) and not b(0)) or
    (a(1) and a(0) and not b(1)) or
    (b(1) and b(0) and cin)) after 10 ns;
END arch;
```

B1-Komplement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
ENTITY b_1komplement IS PORT (
  b: IN STD_LOGIC_VECTOR(1 DOWNTO 0);
  y: OUT STD_LOGIC_VECTOR(1 DOWNTO 0)
);
END b_1komplement;
ARCHITECTURE arch OF b_1komplement IS
BEGIN
y(1) \le (b(1)) after 10 ns;
y(0) \le (\text{not } b(0)) \text{ after } 10 \text{ ns};
END arch;
DMUX:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
ENTITY dmux IS PORT (
  x: IN STD_LOGIC_VECTOR(1 DOWNTO 0);
  y: IN STD LOGIC VECTOR(1 DOWNTO 0);
  s: IN STD_LOGIC;
  Z: OUT STD_LOGIC_VECTOR(1 DOWNTO 0)
);
END dmux;
ARCHITECTURE arch OF dmux IS
BEGIN
z(1) \le ((x(1) \text{ and not s}) \text{ or } (y(1) \text{ and s})) \text{ after 10 ns};
z(0) \le ((x(0) \text{ and not s}) \text{ or } (y(0) \text{ and s})) \text{ after 10 ns};
END arch;
```

```
Primitiv:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
ENTITY primitiv IS PORT (
  a: IN STD_LOGIC_VECTOR(1 DOWNTO 0);
  b: IN STD_LOGIC_VECTOR(1 DOWNTO 0);
  cin: IN STD_LOGIC;
  oper: IN STD LOGIC;
  r: OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
  cout: OUT STD_LOGIC
END primitiv;
ARCHITECTURE arch OF primitiv IS
  SIGNAL i,j: STD_LOGIC_VECTOR(1 DOWNTO 0);
BEGIN
KOMPLEMENT: ENTITY WORK.b 1komplement PORT MAP(b(1 DOWNTO 0), i(1 DOWNTO 0));
MUX: ENTITY WORK.dmux PORT MAP(b(1 DOWNTO 0),i(1 DOWNTO 0), oper, j(1 DOWNTO 0));
ADDER: ENTITY WORK.FA PORT MAP(a(1 DOWNTO 0), j(1 DOWNTO 0), cin, r(1 DOWNTO 0), cout);
END arch;
Zbrajalo:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
ENTITY zbrajalo IS PORT (
  a: IN STD LOGIC VECTOR(7 DOWNTO 0);
  b: IN STD LOGIC VECTOR(7 DOWNTO 0);
  oper: IN STD_LOGIC;
  r: OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
  cout: OUT STD_LOGIC
);
END zbrajalo;
ARCHITECTURE arch OF zbrajalo IS
  SIGNAL i: STD_LOGIC_VECTOR(2 DOWNTO 0);
ADD0: ENTITY WORK.primitiv PORT MAP(a(1 DOWNTO 0), b(1 DOWNTO 0), oper, oper, r(1 DOWNTO
ADD1: ENTITY WORK.primitiv PORT MAP(a(3 DOWNTO 2), b(3 DOWNTO 2), i(0), oper, r(3 DOWNTO
2), i(1));
ADD2: ENTITY WORK.primitiv PORT MAP(a(5 DOWNTO 4), b(5 DOWNTO 4), i(1), oper, r(5 DOWNTO
4), i(2));
ADD3: ENTITY WORK.primitiv PORT MAP(a(7 DOWNTO 6), b(7 DOWNTO 6), i(2), oper, r(7 DOWNTO
6), cout);
END arch:
```