LAB 5 - VERZIJA 2

```
(B-1) komplement
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
ENTITY b1kompl IS PORT(
 x: in std_logic_vector (1 downto 0);
 y: out std_logic_vector (1 downto 0));
end b1kompl;
ARCHITECTURE arch OF b1kompl IS
BEGIN
 y(1) \le not x(1) after 10 ns;
 y(0) \le x(0) after 10 ns;
END arch;
Dvostruki multipleksor
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
ENTITY dmux IS PORT(
 x: in std logic vector (1 downto 0);
 y: in std_logic_vector (1 downto 0);
 s: in std logic;
 z: out std_logic_vector (1 downto 0));
end dmux;
ARCHITECTURE arch OF dmux IS
BEGIN
 z(1) \le (x(1) \text{ and not s}) \text{ or } (y(1) \text{ and s}) \text{ after 10 ns};
 z(0) \le (x(0) \text{ and not s}) \text{ or } (y(0) \text{ and s}) \text{ after 10 ns};
END arch;
```

```
Full Adder
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

ENTITY FA IS PORT(
a: in std_logic_vector (1 downto 0);
b: in std_logic_vector (1 downto 0);
cin: in std_logic;
r: out std_logic_vector (1 downto 0);
cout: out std_logic);
end FA;
```

ARCHITECTURE arch OF FA IS

BEGIN

cout <= ((a(0) and b(1) and not b(0)) or (b(1) and not b(0) and cin) or (not a(1) and a(0) and b(0)) or (a(1) and not a(0) and b(1)) or (a(1) and not a(0) and b(0)) or (a(1) and not a(0) and b(0)) or (a(1) and not a(0) and cin) or (a(1) and not b(1) and b(0)) and (a(1) and not b(1) and b(0)) or (a(1) and not b(1) and not b(1)) or (a(1) and not b(1) and not b(1)) or (a(1) and not b(1

 $r(1) \le (\text{(not a(1) and b(1) and not cin)})$ or (not a(1) and not b(1) and cin) or (a(1) and not b(1)) and (a(1) and not b(1)) or (a(1) and not b(1)) and $(\text{a(1) and n$

 $r(0) \le (a(0) \text{ and } b(1) \text{ and not } b(0) \text{ and cin})$ or (not a(0) and b(1) and b(0) and cin) or (a(1) and a(0) and not b(1) and b(0)) or (not a(1) and a(0) and not b(0) and not cin) or (not a(1) and not a(0) and b(0) and not cin) or (a(1) and a(0) and b(1) and b(0) and not cin) or (not a(1) and a(0) and not b(1) and b(0) and cin) or (a(1) and not a(0) and not b(1) and not b(0) and cin) or (not a(1) and not a(0) and not b(1) and not b(0) and not b(0) and cin) or (not a(1) and not a(0) and not b(1) and not b(0) and not b(0)

END arch;

```
Primitiv
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
ENTITY primitiv IS PORT(
 a: in std_logic_vector (1 downto 0);
 b: in std_logic_vector (1 downto 0);
 cin: in std logic;
 oper: in std_logic;
 r: out std_logic_vector (1 downto 0);
 cout : out std_logic);
end primitiv;
ARCHITECTURE arch OF primitiv IS
 SIGNAL i,j: std_logic_vector (1 downto 0);
BEGIN
 b1kompl : ENTITY work.b1kompl PORT MAP (b, i);
 dmux: ENTITY work.dmux PORT MAP (b, i, oper, j);
 FA: ENTITY work.FA PORT MAP (a, j, cin, r, cout);
```

END arch;

```
Zbrajalo
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
ENTITY zbrajalo IS PORT(
 a: in std_logic_vector (7 downto 0);
 b: in std_logic_vector (7 downto 0);
 oper: in std logic;
 r : out std_logic_vector (7 downto 0);
 cout: out std logic);
end zbrajalo;
ARCHITECTURE arch OF zbrajalo IS
 SIGNAL c : std_logic_vector (2 downto 0);
BEGIN
 prim1: ENTITY work.primitiv PORT MAP (a(1 downto 0), b(1 downto 0), oper, oper, r(1
 downto 0), c(0));
 prim2: ENTITY work.primitiv PORT MAP (a(3 downto 2), b(3 downto 2), c(0), oper, r(3 downto
 2), c(1));
 prim3: ENTITY work.primitiv PORT MAP (a(5 downto 4), b(5 downto 4), c(1), oper, r(5 downto
 prim4: ENTITY work.primitiv PORT MAP (a(7 downto 6), b(7 downto 6), c(2), oper, r(7 downto
 6), cout);
END arch;
```